

Roll No.

Total No. of Questions : 09]

[Total No. of Pages : 02

B.Tech. (Sem. - 3rd)

ELECTRONIC DEVICES AND CIRCUITS

SUBJECT CODE : EC - 201

Paper ID : [A0301]

[Note : Please fill subject code and paper ID on OMR]

Time : 03 Hours

Maximum Marks : 60

Instruction to Candidates:

- 1) Section - A is **Compulsory**.
- 2) Attempt any **Four** questions from Section - B.
- 3) Attempt any **Two** questions from Section - C.

Section - A

Q1)

(10 × 2 = 20)

- a) What will be the PIV of non-conducting diode if V_m is the peak voltage across secondary of the transformer in a half-wave rectifier and a shunt capacitor filter is also used?
- b) Write any two applications of Photo diode.
- c) What are characteristics of a good amplifier?
- d) In what respect FETs better than BJTs?
- e) Define photosensitivity of a photo transistor.
- f) What happens to the drain current of a n-channel JFET when a negative voltage is applied on its gate?
- g) Why it is always considered better to fix Q-point in the middle of active region?
- h) Explain why fixed bias circuit, inspite of its simplicity, is not much used in practice?
- i) Define $h_{12} = \frac{v_1}{i=0}$
 v_2
- j) Why common collector amplifier called emitter follower?

Section - B

(4 × 5 = 20)

- Q2) Show that rectification efficiency for a half wave rectifier is 40.6%?
- Q3) What is LCD? Discuss its advantages, disadvantages and applications?
- Q4) Explain with equivalent circuit working of Photo transistor.
- Q5) Discuss determination of h-parameters from transistor characteristics.
- Q6) Describe construction, working and characteristics of n-channel JFET?

Section - C

(2 × 10 = 20)

- Q7) a) Why there is a need for bias stabilization?
b) Explain working of Voltage divider bias circuit.
- Q8) a) Discuss analysis of transistor amplifier using h-parameter in CB configuration?
b) What will be the effect of an emitter bypass capacitor on frequency response of an amplifier?
- Q9) Describe analysis of emitter follower using Miller's theorem?

